06/02/16 06:05:11 C:\Users\Danish\Files\Dropbox\College\2nd Year\Q3\ECE 152A\Lab #3\finalCode.v

```
//Danish Vaid, Dylan Goldsworthy, Anubhav Basak
   //What the code does:
   //This code is written to create the circuit for a Ford Thunderbird
5
   //tail light controller
   //Inputs: clk, reset, brake, hazard, left, right [listed in our files as x0x1x2x3x4]
6
   //Ouputs: Lc, Lb, La, Ra, Rb, Rc
8
   //-----
9
10
   // Main Function
   11
   module tailLightControllerMain(dimClk, lights, clk, reset, brake, hazard, left, right, Lc, Lb, La, Ra, Rb, Rc);
12
13
   input dimClk, lights, clk, reset, brake, hazard, left, right;
   output Lc, Lb, La, Ra, Rb, Rc;
14
                           //Temp Memory Storage
15
   wire[2:0] Lcba;
   wire[2:0] Rabc;
16
   tailLightControllerStateMachine f1(clk, reset, brake, hazard, left, right, Lcba, Rabc);
17
   tailLightControllerDimmer d1(dimClk, lights, Lcba, Rabc, Lc, Lb, La, Ra, Rb, Rc);
18
   endmodule
19
    //-----
20
21
    // Controls when the lights get checked for dim or not
22
   //-----
   module tailLightControllerDimmer(input dimClk, input lights, input[2:0] Lcba, input[2:0] Rabc, output reg Lc, output reg Lb,
23
   output reg La, output reg Ra, output reg Rb, output reg Rc);
24
   req toggle;
                        //Dimming Helper
   always@(posedge dimClk ) begin
25
   if(lights) begin
26
   toggle <= ~toggle;</pre>
27
28
   if(Lcba[2]) begin
29
30
   Lc = 1'b1;
31
   end
32
   else begin
33
   Lc = toggle;
34
   end
35
   if(Lcba[1]) begin
36
37
   Lb = 1'b1;
38
   end
39
   else begin
40
   Lb = toggle;
41
   end
42
43
   if(Lcba[0]) begin
44
   La = 1'b1;
45
   end
46
   else begin
47
   La = toggle;
48
   end
49
50
   if(Rabc[1]) begin
51
   Ra = 1'b1;
52
   end
53
   else begin
54
   Ra = toggle;
55
   end
56
57
   if(Rabc[1]) begin
   Rb = 1'b1;
58
59
   end
60
   else begin
61
   Rb = toggle;
62
   end
63
64
   if(Rabc[0]) begin
65
   Rc = 1'b1;
66
   end
67
   else begin
68
   Rc = toggle;
69
   end
70
71
   end
   else begin
72
73
   Lc = Lcba[2];
74
   Lb = Lcba[1];
75
   La = Lcba[0];
   Ra = Rabc[2];
76
   Rb = Rabc[1];
77
78
   Rc = Rabc[0];
79
   end
80
   end
81
   endmoduLe
```

6/2/2016 finalCode.v

```
83
84
    // State machine for the circuit
85
    module tailLightControllerStateMachine(input clk, input reset, input brake, input hazard, input left, input right, output
86
    reg[2:0] Lcba, output reg[2:0] Rabc);
87
88
    // Local Parameters All possible states
    //-----
89
     `define state_off 4'd0
90
91
     define state_brake 4'd1
92
     define state_l1 4'd2
93
     define state_12
                    4'd3
                   4'd4
94
     `define state_13
95
     `define state_r1
                   4'd5
96
     `define state_r2
                    4'd6
97
     `define state r3
                   4'd7
     define state_bl1 4'd8
define state_bl2 4'd9
98
99
     define state_bl2
100
    `define state_br1 4'd10
101
     define state_br2 4'd11
102
     `define state_hazard 4'd12
103
    //-----
104
    // Registry States
105
    //----
106
    reg[3:0] currentState; //Current state value
107
    reg[3:0] nextState;
                              //Next state value
108
    //----
109
    // Outputs
110
    //-----
    always@( * ) begin
111
112
    case(currentState)
113
     `state_off: begin
       Lcba = 3'b000;
                             //Can change to be Lc = 1_b0
114
       Rabc = 3'b000;
115
116
117
        state brake: begin
       Lcba = 3'b111;
118
119
       Rabc = 3'b111;
120
       end
121
        `state_l1: begin
       Lcba = 3'b001;
Rabc = 3'b000;
122
123
124
       end
125
        `state_12: begin
       Lcba = 3'b011;
126
       Rabc = 3'b000;
127
128
       end
        `state_13: begin
129
       Lcba = 3'b111;
130
       Rabc = 3'b000;
131
132
       end
133
        `state_r1: begin
       Lcba = 3'b000;
134
       Rabc = 3'b100;
135
136
       end
137
        `state_r2: begin
       Lcba = 3'b000;
138
       Rabc = 3'b110;
139
140
        end
141
        `state_r3: begin
142
       Lcba = 3'b000;
       Rabc = 3'b111;
143
144
       end
145
        `state_bl1: begin
       Lcba = 3'b001;
146
       Rabc = 3'b111;
147
148
        end
149
        state_bl2: begin
       Lcba = 3'b011;
150
       Rabc = 3'b111;
151
152
       end
153
        state_br1: begin
154
       Lcba = 3'b111;
       Rabc = 3'b100;
155
156
       end
157
        `state_br2: begin
       Lcba = 3'b111;
158
       Rabc = 3'b110;
159
160
       end
161
        state_hazard: begin
162
       Lcba = 3'b111;
163
       Rabc = 3'b111;
164
       end
165
       endcase
```

6/2/2016 finalCode.v

```
//-----
167
168
     // Change Current to Next State
     //----
169
170
     always@(posedge clk) begin
     if(reset) currentState <= `state_off;</pre>
171
172
     else currentState <= nextState;</pre>
173
174
     //----
     // Next State Selector [xxxxx]
175
176
177
     always@( * ) begin
     nextState = currentState;
178
       if(reset) begin
                                       //If 1xxxx
179
180
        nextState = `state_off;
181
        else if(!reset && brake && !left && !right) begin
                                                             //If 01x00
182
        nextState = `state_brake;
183
184
        end
        else if(!reset && brake && left && right) begin
185
186
        nextState = `state brake;
187
188
        else if(!reset && !brake && hazard && (currentState != `state_hazard)) begin
189
         nextState = `state_hazard;
190
         else if(!reset && !brake && !hazard && left && right && (currentState != `state_hazard)) begin
191
192
         nextState = `state_hazard;
                                                //If 00011
193
194
        else if(!reset && !brake && !hazard && !left && !right) begin //If 00000
195
        nextState = `state off;
196
        end
197
        else begin
198
        case (currentState)
199
          `state_off: begin
                                          //state_off
          if(!reset && brake && !left && right) nextState = `state_br1;
200
          if(!reset && brake && left && !right) nextState = `state_bl1;
201
202
          if(!reset && !brake && !hazard && left && !right) nextState = `state l1;
          if(!reset && !brake && !hazard && !left && right) nextState = `state_r1;
203
204
          end
205
          state_brake: begin
206
          if(!reset && brake && !left && right) nextState = `state_br1;
          if(!reset && brake && left && !right) nextState = `state_bl1;
207
          if(!reset && !brake && !hazard && left && !right) nextState = `state_11;
208
          if(!reset && !brake && !hazard && !left && right) nextState = `state_r1;
209
210
          end
          `state l1: begin
211
          if(!reset && brake && !left && right) nextState = `state_br1;
if(!reset && brake && left && !right) nextState = `state_bl2;
212
213
          if(!reset && !brake && !hazard && left && !right) nextState = `state_12;
214
          if(!reset && !brake && !hazard && !left && right) nextState = `state_r1;
215
216
          end
217
          state_12: begin
          if(!reset && brake && !left && right) nextState = `state_br1;
218
          if(!reset && brake && left && !right) nextState = `state_brake;
219
220
          if(!reset && !brake && !hazard && left && !right) nextState = `state_13;
          if(!reset && !brake && !hazard && !left && right) nextState = `state_r1;
221
222
          end
223
          state_13: begin
          if(!reset && brake && !left && right) nextState = `state_br1;
224
          if(!reset && brake && left && !right) nextState = `state_r3;
225
226
          if(!reset && !brake && !hazard && left && !right) nextState = `state_off;
227
          if(!reset && !brake && !hazard && !left && right) nextState = `state r1;
228
          end
229
          state_r1: begin
230
          if(!reset && brake && !left && right) nextState = `state_br2;
          if(!reset && brake && left && !right) nextState = `state_bl1;
231
          if(!reset && !brake && !hazard && left && !right) nextState = `state_l1;
232
          if(!reset && !brake && !hazard && !left && right) nextState = `state_r2;
233
234
235
          `state_r2: begin
          if(!reset && brake && !left && right) nextState = `state_brake;
if(!reset && brake && left && !right) nextState = `state_bl1;
236
237
          if(!reset && !brake && !hazard && left && !right) nextState = `state_l1;
238
          if(!reset && !brake && !hazard && !left && right) nextState = `state_r3;
239
240
          end
241
          state r3: begin
          if(!reset && brake && !left && right) nextState = `state_13;
if(!reset && brake && left && !right) nextState = `state_bl1;
242
243
          if(!reset && !brake && !hazard && left && !right) nextState = `state 11;
244
          if(!reset && !brake && !hazard && !left && right) nextState = `state_off;
245
246
          end
247
          state_bl1: begin
248
          if(!reset && brake && !left && right) nextState = `state_br1;
          if(!reset && brake && left && !right) nextState = `state_bl2;
249
          if(!reset && !brake && !hazard && left && !right) nextState = `state_12;
250
          if(!reset && !brake && !hazard && !left && right) nextState = `state_r1;
```

6/2/2016 finalCode.v

```
252
            end
253
             state_bl2: begin
            if(!reset && brake && !left && right) nextState = `state_br1;
254
            if(!reset && !brake && !left && !right) nextState = `state_brake;
if(!reset && !brake && !hazard && !eft && !right) nextState = `state_la;
if(!reset && !brake && !hazard && !left && right) nextState = `state_l3;
if(!reset && !brake && !hazard && !left && right) nextState = `state_r1;
255
256
257
258
            end
259
             `state_br1: begin
            if(!reset && brake && !left && right) nextState = `state_br2;
if(!reset && brake && left && !right) nextState = `state_bl1;
260
261
262
            if(!reset && !brake && !hazard && left && !right) nextState = `state_11;
263
            if(!reset && !brake && !hazard && !left && right) nextState = `state_r2;
264
            end
265
             `state_br2: begin
266
            if(!reset && brake && !left && right) nextState = `state_brake;
            if(!reset && brake && left && !right) nextState = `state_bl1;
267
            if(!reset && !brake && !hazard && left && !right) nextState = `state_l1;
268
269
            if(!reset && !brake && !hazard && !left && right) nextState = `state_r3;
270
271
             state_hazard: begin
            if(!reset && brake && !left && right) nextState = `state_br1;
if(!reset && brake && left && !right) nextState = `state_bl1;
272
273
274
            if(!reset && !brake && !hazard && left && !right) nextState = `state_11;
            if(!reset && !brake && !hazard && !left && right) nextState = `state_r1;
if(!reset && !brake && hazard) nextState = `state_off;
275
276
            if(!reset && !brake && !hazard && left && right) nextState = `state_off;
277
278
279
            //default: nextState = state_off;
                                                              //Not sure whether to implement
280
281
            endcase
282
            end
283
            end
284
            endmodule
```